

Introduction to VLSI

Lab 4

By:

*Rebecca Curtis
Kancy Robinson
David Zemon
Eric Pyle
Will Roussin*


Table of Contents

AND.....	4
Layout.....	4
Specifications.....	4
LVS.....	4
NAND.....	5
Layout.....	5
Specifications.....	5
LVS.....	6
OR.....	7
Layout.....	7
Specifications.....	7
LVS.....	7
NOR.....	8
Layout.....	8
Specifications.....	8
LVS.....	9
XNOR.....	10
Layout.....	10
Specifications.....	10
LVS.....	10
XOR.....	11
Layout.....	11
Specifications.....	11
LVS.....	11
4-Input AND.....	12
Layout.....	12
Specifications.....	12
LVS.....	13
Post Layout Simulation.....	14
4-Input OR.....	14
Layout.....	14
Specifications.....	14
LVS.....	15
Post Layout Simulation.....	16
4-Input XNOR.....	16
Layout.....	16
Specifications.....	17
LVS.....	17
Post Layout Simulation.....	18
4-Input XOR.....	19
Layout.....	19
Specifications.....	19
LVS.....	19
Post Layout Simulation.....	21

1-bit Full Adder.....	21
Layout.....	21
Specifications.....	22
LVS.....	22
Post Layout Simulation.....	23
4-bit Adder/Subtractor.....	23
Layout.....	23
Specifications.....	23
LVS.....	23
Post Layout Simulation.....	25

AND

Layout

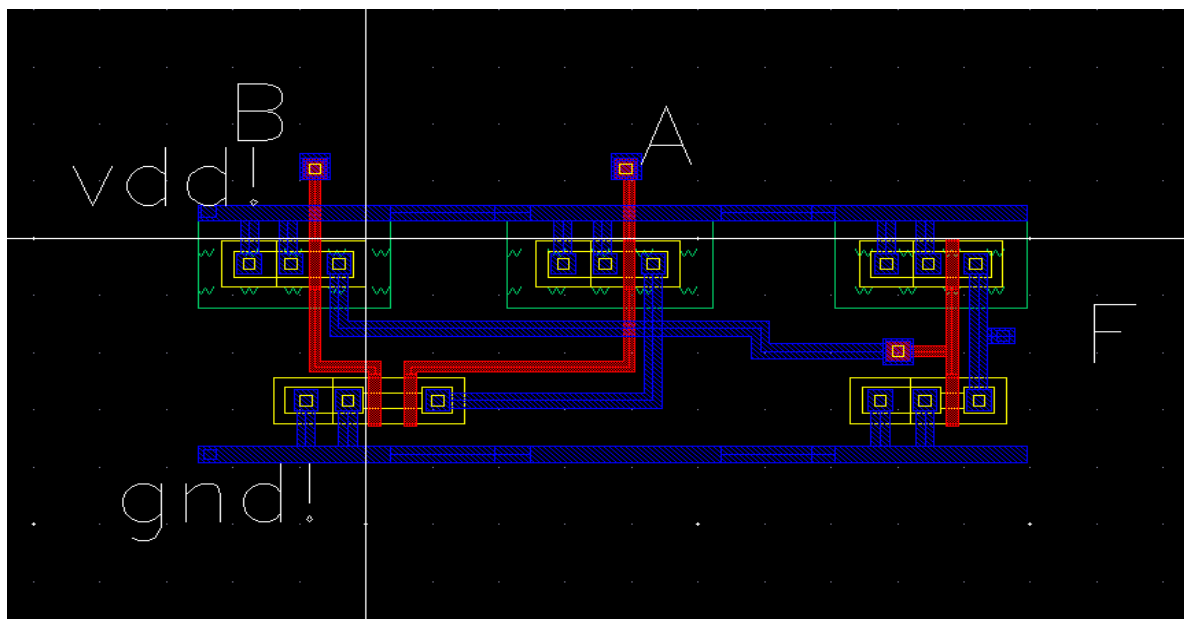

Specifications

Total Area: $A = 4.5 \mu\text{m} \times 12.465 \mu\text{m} = 56.093 \mu\text{m}^2$

Power Consumption: $P = 40 \text{ mA} \cdot 2.2 \text{ V} + 31 \text{ mA} \cdot 2.2 \text{ V} = 75 \text{ mW}$

LVS

Compiling Diva LVS rules...

Net-list summary for /tmp/davidzGit/project/and/LVS/layout/netlist

count	
7	nets
5	terminals
3	pmos
3	nmos

Net-list summary for /tmp/davidzGit/project/and/LVS/schematic/netlist

count	
7	nets
5	terminals
3	pmos
3	nmos

Terminal correspondence points

N5	N3	A
N4	N2	B
N3	N5	F
N2	N1	gnd!
N6	N0	vdd!

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:


cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	6	6
total	6	6
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	7	7
total	7	7
	terminals	
un-matched	0	0
matched but different type	1	1
total	5	5

NAND

Layout

 

Specifications

Total Area: $A = 4.86 \mu m \times 9.0 \mu m = 43.74 \mu m^2$

Power consumption: $P = 334.3 \mu A \cdot 1.8 V + 41.31 \mu A \cdot 1.8 V = 676.098 mW$

LVS

Compiling Diva LVS rules...

Net-list summary for /tmp/davidzGit/project/nand/LVS/layout/netlist

count	
6	nets
5	terminals
2	pmos
2	nmos

Net-list summary for /tmp/davidzGit/project/nand/LVS/schematic/netlist

count	
6	nets
5	terminals
2	pmos
2	nmos

Terminal correspondence points

N4	N7	A
N3	N2	B
N2	N6	F
N1	N1	gnd!
N5	N0	vdd!

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:


cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	4	4
total	4	4
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	6	6
total	6	6
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	5	5

OR

Layout

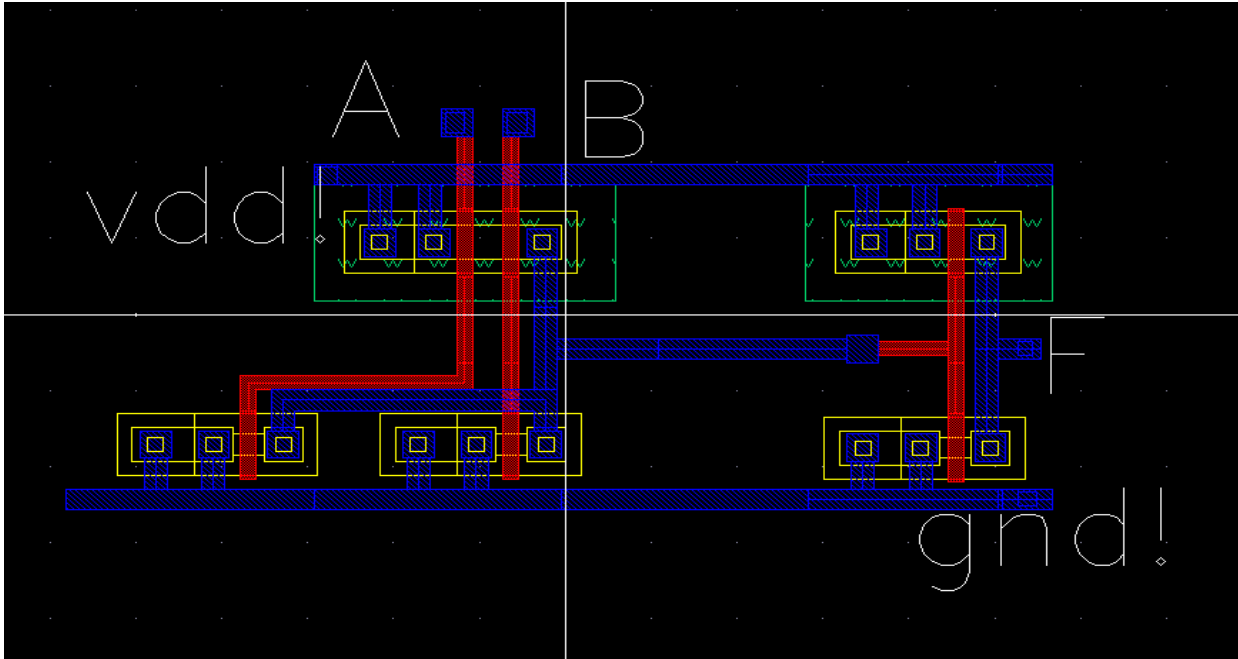

Specifications

Total Area: $A = 4.545 \mu m \times 11.475 \mu m = 52.154 \mu m^2$

Power Consumption: $P = 89.97 \mu A \cdot 1.8 V + 560.97 \mu A \cdot 1.8 V = 1,171.692 mW$

LVS

Compiling Diva LVS rules...

Net-list summary for /tmp/davidzGit/project/or/LVS/layout/netlist

count	
7	nets
5	terminals
3	pmos
3	nmos

Net-list summary for /tmp/davidzGit/project/or/LVS/schematic/netlist

count	
7	nets
5	terminals
3	pmos
3	nmos

Terminal correspondence points

N5	N2	A
N4	N5	B
N3	N3	F
N2	N0	gnd!
N6	N1	vdd!

Devices in the rules but not in the netlist:


cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	6	6
total	6	6
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	7	7
total	7	7
	terminals	
un-matched	0	0
matched but different type	0	0
total	5	5

NOR

Layout:

 

Specifications

Total Area: $A = 5.265 \mu\text{m} \times 7.245 \mu\text{m} = 38.145 \mu\text{m}^2$

Power Consumption: $P = 532.08 \mu\text{A} \cdot 1.8 \text{ V} + 87.703 \mu\text{A} \cdot 1.8 \text{ V} = 1,115.609 \text{ mW}$

LVS

Compiling Diva LVS rules...

Net-list summary for /tmp/davidzGit/project/nor/LVS/layout/netlist

count	
6	nets
5	terminals
2	pmos
2	nmos

Net-list summary for /tmp/davidzGit/project/nor/LVS/schematic/netlist

count	
6	nets
5	terminals
2	pmos
2	nmos

Terminal correspondence points

N4	N7	A
N3	N5	B
N2	N2	F
N1	N1	gnd!
N5	N0	vdd!

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:


cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	4	4
total	4	4
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	6	6
total	6	6
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	5	5

XNOR

Layout

 

Specifications

Total Area: $A = 12.825 \mu\text{m} \times 33.795 \mu\text{m} = 433.421 \mu\text{m}^2$

Power Consumption: $P = 665.82 \mu\text{A} \cdot 1.8 \text{V} = 1,198.476 \text{mW}$

LVS

Compiling Diva LVS rules...

```
Net-list summary for /tmp/davidzGit/project/xnor/LVS/layout/netlist
count
16      nets
5        terminals
12      pmos
12      nmos
```

```
Net-list summary for /tmp/davidzGit/project/xnor/LVS/schematic/netlist
count
16      nets
5        terminals
12      pmos
12      nmos
```

Terminal correspondence points

N14	N3	A
N13	N5	B
N12	N4	F
N11	N0	gnd!
N15	N1	vdd!

Devices in the netlist but not in the rules:
pcapacitor


Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	24	24
total	24	24
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	16	16
total	16	16
	terminals	
un-matched	0	0
matched but different type	0	0
total	5	5

XOR

Layout

 

Specifications

Total Area: $34.11\ \mu\text{m} \times 12.375\ \mu\text{m} = 422.111\ \mu\text{m}^2$
Power Consumption: $P = 666.48\ \mu\text{A} \cdot 1.8\ \text{V} = 1,199.664\ \mu\text{W}$

LVS

Compiling Diva LVS rules...	
Net-list summary for /tmp/davidzGit/project/xor/LVS/layout/netlist	
count	
15	nets
5	terminals
11	pmos
11	nmos
Net-list summary for /tmp/davidzGit/project/xor/LVS/schematic/netlist	
count	
15	nets

```

5          terminals
11         pmos
11         nmos

```

Terminal correspondence points

```

N13      N6      A
N12      N7      B
N11      N3      F
N10      N1      gnd!
N14      N0      vdd!

```

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:


cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	22	22
total	22	22
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	15	15
total	15	15
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	5	5

4-Input AND

Layout

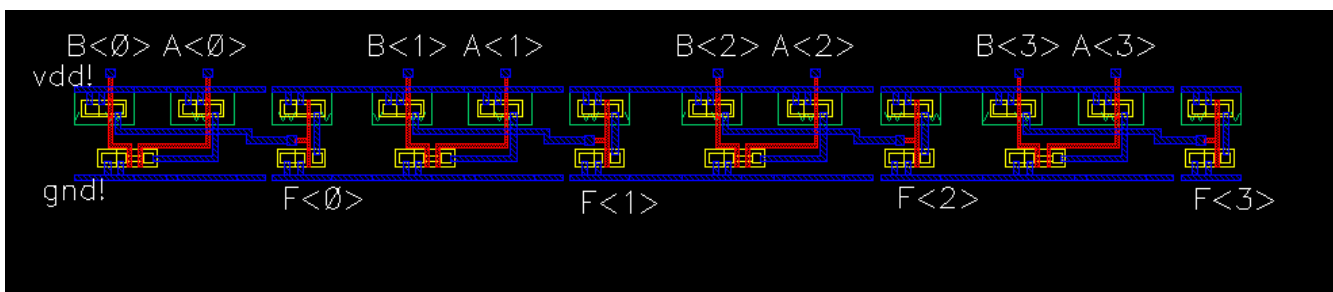

Specifications

Total Area: $A = 5.49 \mu m \times 56.385 \mu m = 309.554 \mu m^2$

Power Consumption: $P = 343.76 \mu A \cdot 1.8 V + 359.4 \mu A \cdot 1.8 V + 349.56 \mu A \cdot 1.8 V = 1,959.3432 \mu W$

LVS

Compiling Diva LVS rules...

Net-list summary for /tmp/davidzGit/project/4bit_and/LVS/layout/netlist

```

count
22      nets
14      terminals
12      pmos
12      nmos

```

Net-list summary for /tmp/davidzGit/project/4bit_and/LVS/schematic/netlist

```

count
22      nets
14      terminals
12      pmos
12      nmos

```

Terminal correspondence points

```

N15      N10      A<0>
N13      N12      A<1>
N11      N13      A<2>
N8       N11      A<3>
N20      N6       B<0>
N18      N8       B<1>
N17      N9       B<2>
N16      N7       B<3>
N12      N3       F<0>
N9       N2       F<1>
N21      N4       F<2>
N19      N5       F<3>
N10      N1       gnd!
N14      N0       vdd!

```

Devices in the netlist but not in the rules:

pcapacitor


Devices in the rules but not in the netlist:

cap nfet pfet nmos4 pmos4

The net-lists match.


	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	24	24
total	24	24
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	22	22
total	22	22
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	14	14

Post Layout Simulation

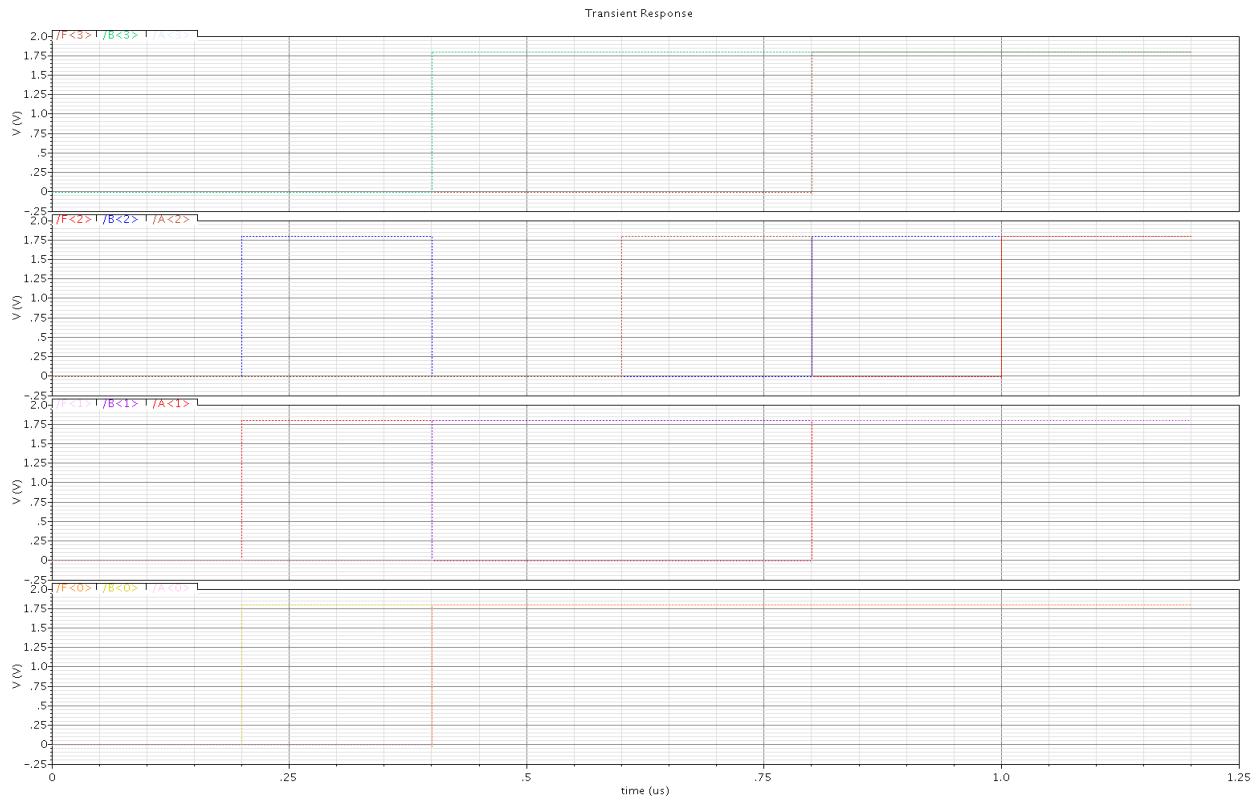

4-Input OR

Layout

 

Specifications

Total Area: $A = 4.54 \mu m \times 37.035 \mu m = 168.139 \mu m^2$

Power Consumption: $P = -7.835 \mu A \cdot 1.8 V + 778.04 \mu A \cdot 1.8 V + 776.5 \mu A \cdot 1.8 V = 2,785.572 \mu W$

LVS

Compiling Diva LVS rules...

Net-list summary for /tmp/davidzGit/project/4bit_or/LVS/layout/netlist

count	
22	nets
14	terminals
12	pmos
12	nmos

Net-list summary for /tmp/davidzGit/project/4bit_or/LVS/schematic/netlist

count	
22	nets
14	terminals
12	pmos
12	nmos

Terminal correspondence points

N15	N8	A<0>
N13	N9	A<1>
N11	N10	A<2>
N8	N3	A<3>
N20	N11	B<0>
N18	N4	B<1>
N17	N5	B<2>
N16	N12	B<3>
N12	N7	F<0>
N9	N13	F<1>
N21	N2	F<2>
N19	N6	F<3>
N10	N0	gnd!
N14	N1	vdd!

Devices in the netlist but not in the rules:

pcapacitor


Devices in the rules but not in the netlist:

cap nfet pfet nmos4 pmos4

The net-lists match.


	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	24	24
total	24	24
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	22	22
total	22	22
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	14	14

Post Layout Simulation

 

4-Input XNOR

Layout

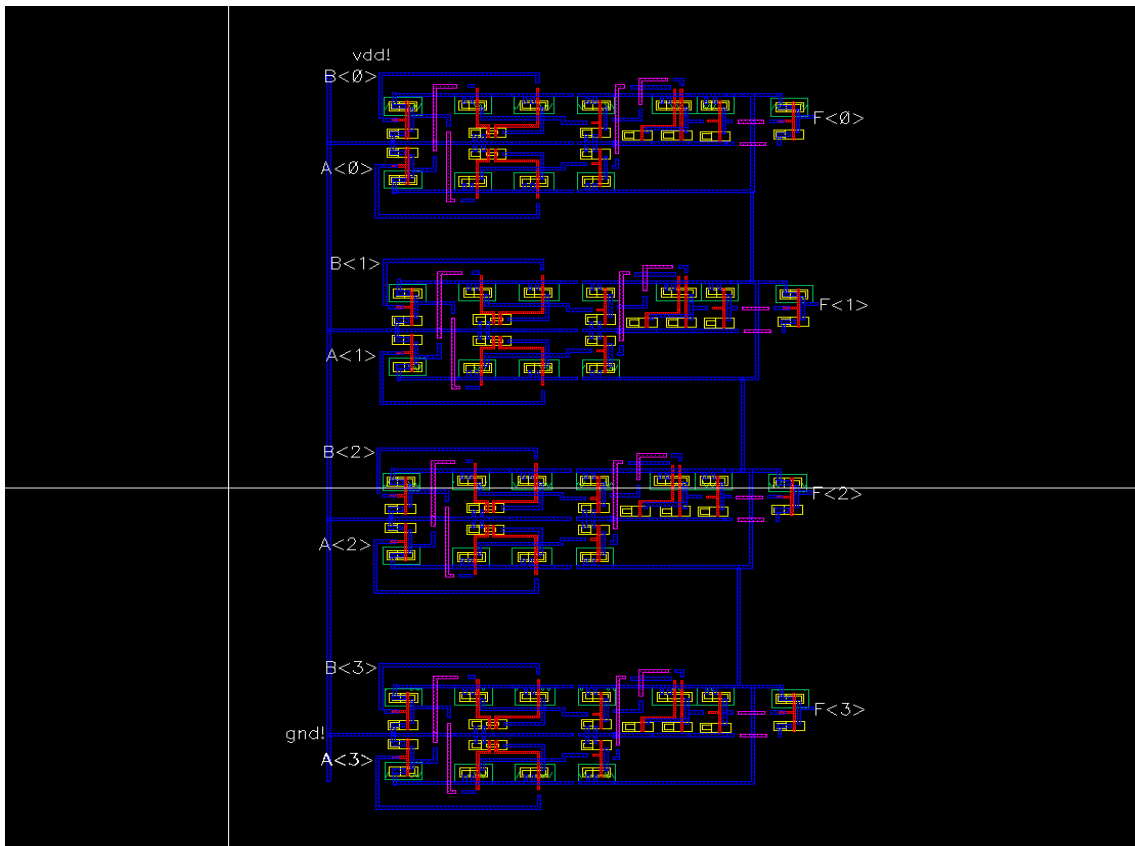

Specifications

Total Area: $A = 38.07 \mu m \times 64.53 \mu m = 2,456.657 \mu m^2$

Power Consumption:

$$P = 712.66 \mu A \cdot 1.8 V + 626.39 \mu A \cdot 1.8 V + 604.03 \mu A \cdot 1.8 V + 665.62 \mu A \cdot 1.8 V = 4,695.66 \mu W$$

LVS

Compiling Diva LVS rules...

Net-list summary for /tmp/davidzGit/project/4b_xnor/LVS/layout/netlist

count	
58	nets
14	terminals
48	pmos
48	nmos

Net-list summary for /tmp/davidzGit/project/4b_xnor/LVS/schematic/netlist

count	
58	nets
14	terminals
48	pmos
48	nmos

Terminal correspondence points

N50	N2	A<0>
N49	N3	A<1>
N47	N4	A<2>
N44	N5	A<3>
N56	N6	B<0>
N54	N7	B<1>
N53	N8	B<2>
N52	N9	B<3>
N48	N10	F<0>
N45	N11	F<1>
N57	N12	F<2>
N55	N13	F<3>
N46	N0	gnd!
N51	N1	vdd!


Devices in the netlist but not in the rules:
pcapacitor

Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.


	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	96	96
total	96	96
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	58	58
total	58	58
	terminals	
un-matched	0	0
matched but different type	0	0
total	14	14

Post Layout Simulation

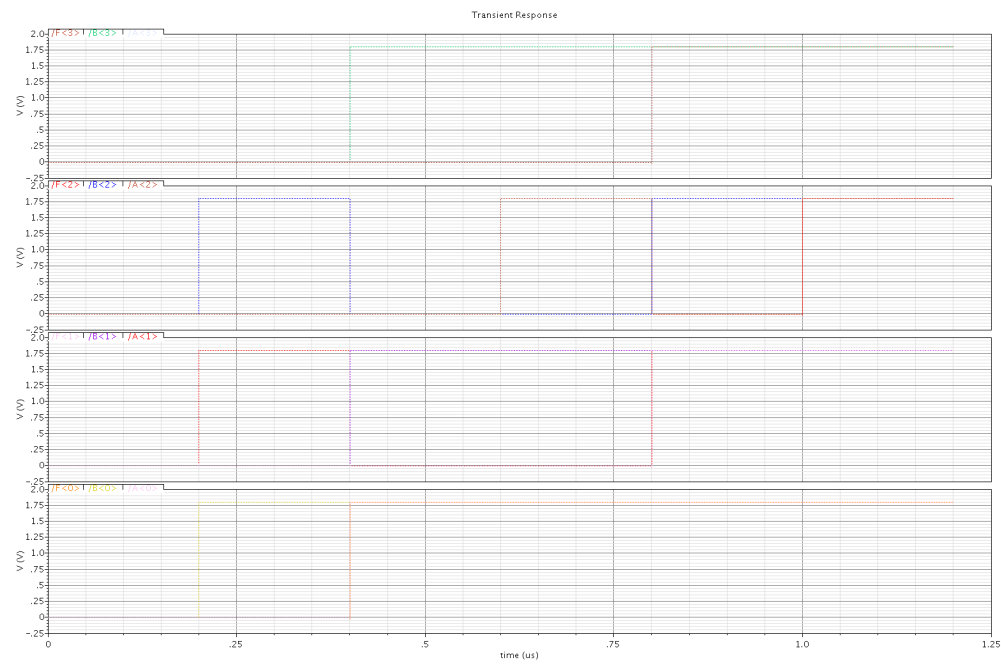

4-Input XOR

Layout

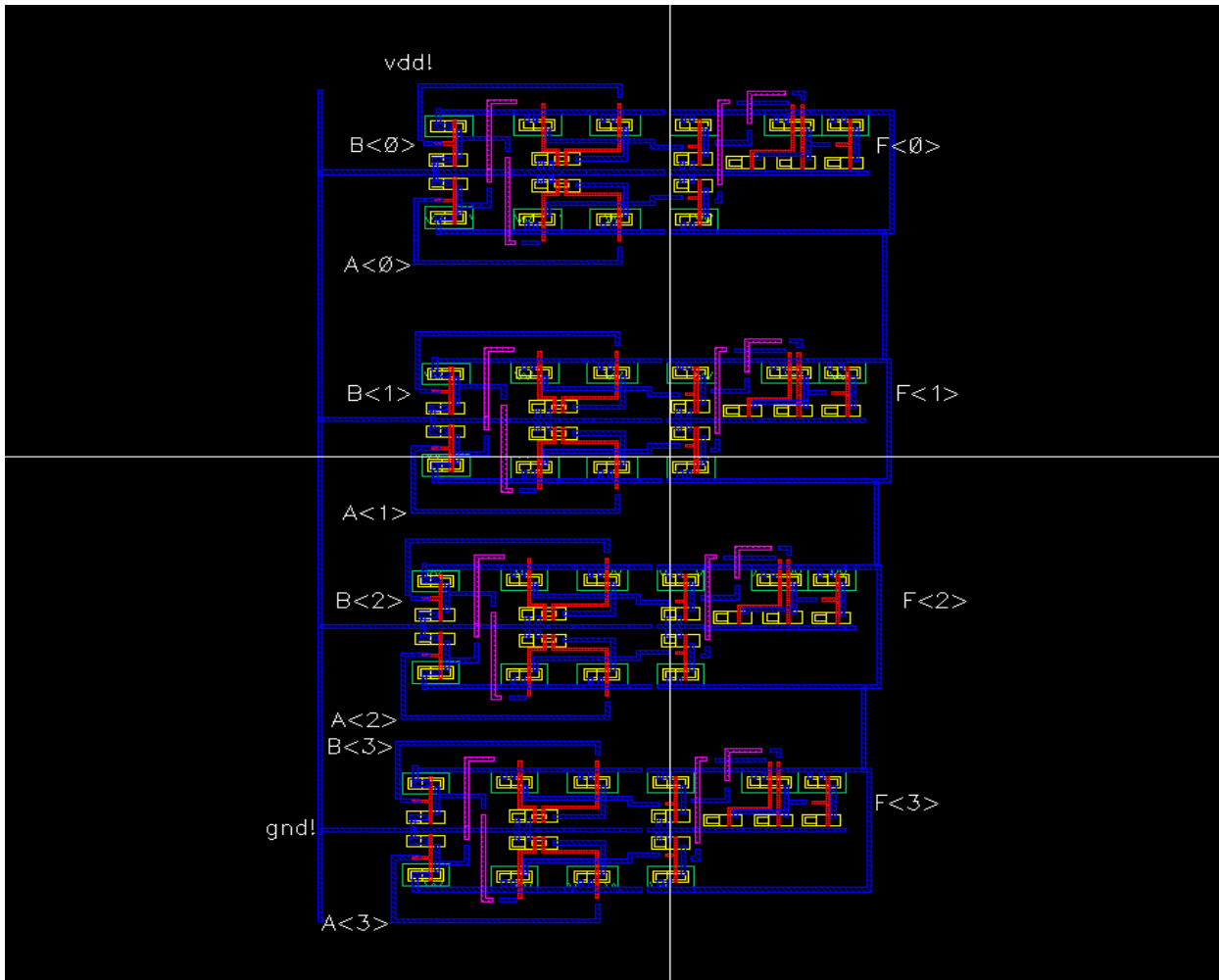

Specifications

Total Area: $A = 33.975 \mu\text{m} \times 59.04 \mu\text{m} = 2,005.884 \mu\text{m}^2$

Power Consumption: $P = 602.94 \mu\text{A} \cdot 1.8 \text{ V} = 1,085.292 \mu\text{W}$

LVS

Compiling Diva LVS rules...

```
Net-list summary for /tmp/davidzGit/project/4bit_xor/LVS/layout/netlist
count
  54      nets
  14      terminals
  44      pmos
  44      nmos
```

```
Net-list summary for /tmp/davidzGit/project/4bit_xor/LVS/schematic/netlist
count
  54      nets
```

```

14      terminals
44      pmos
44      nmos

```

Terminal correspondence points

```

N46      N3      A<0>
N45      N4      A<1>
N43      N2      A<2>
N40      N13     A<3>
N52      N8      B<0>
N50      N7      B<1>
N49      N6      B<2>
N48      N5      B<3>
N44      N9      F<0>
N41      N10     F<1>
N53      N11     F<2>
N51      N12     F<3>
N42      N1      gnd!
N47      N0      vdd!

```


Devices in the netlist but not in the rules:
pcapacitor

Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.


	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	88	88
total	88	88
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	54	54
total	54	54
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	14	14

Post Layout Simulation

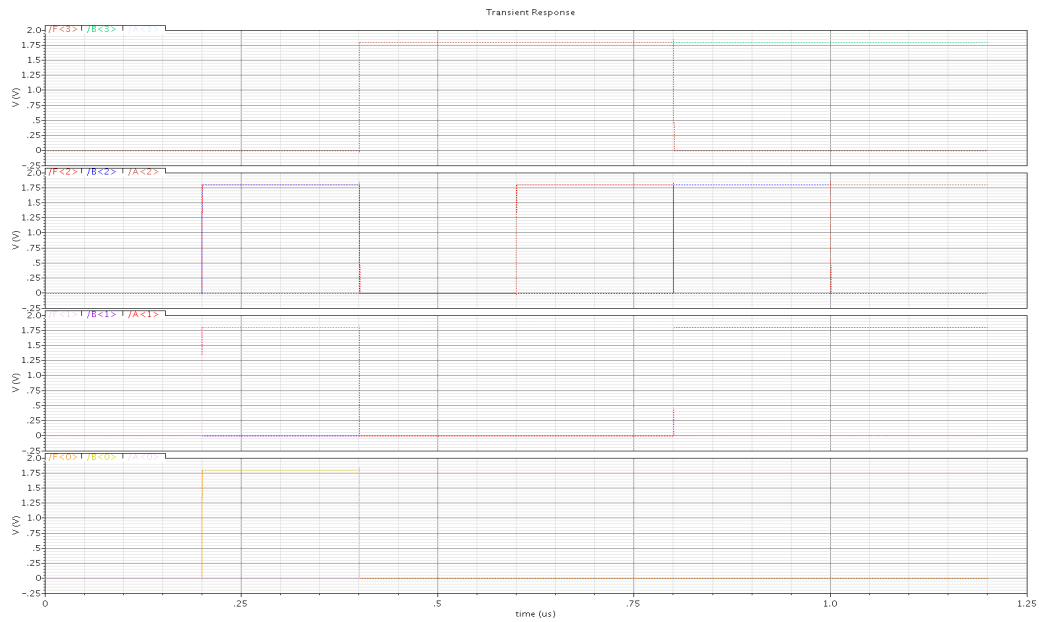

1-bit Full Adder

Layout

 

Specifications

Total Area: $A = 54.855 \mu\text{m} \times 31.95 \mu\text{m} = 1752.617 \mu\text{m}^2$

Power Consumption:

LVS

Compiling Diva LVS rules...

Net-list summary for /tmp/davidzGit/project/lb_fullAdder/LVS/layout/netlist

count	
36	nets
5	terminals
31	pmos
31	nmos

Net-list summary for /tmp/davidzGit/project/lb_fullAdder/LVS/schematic/netlist

count	
36	nets
7	terminals
31	pmos
31	nmos

Terminal correspondence points

N35	N2	A
N34	N9	B
N33	N4	Ci
N32	N6	Co
N31	N8	S

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:

cap nfet pfet nmos4 pmos4


The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	62	62
total	62	62
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	36	36
total	36	36
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	5	7

Post Layout Simulation

4-bit Adder/Subtractor

Layout

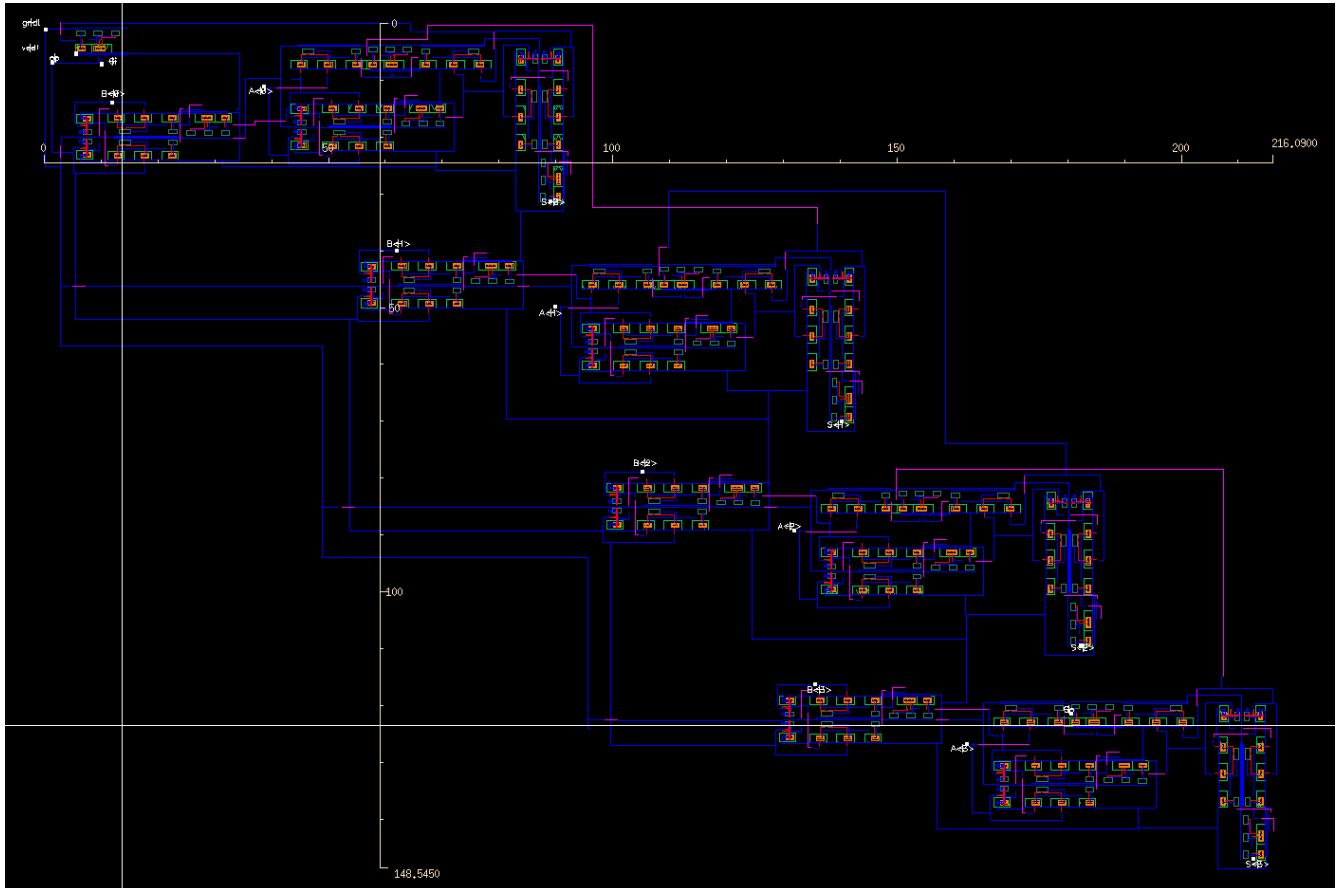

Specifications

Total Area: $A = 217.395 \mu m \times 149.31 \mu m = 32,459.247 \mu m^2$

Power Consumption:

LVS

Compiling Diva LVS rules...

```
Net-list summary for /tmp/davidzGit/project/4b_adder_subtractor/LVS/layout/netlist
count
183      nets
17       terminals
171      pmos
171      nmos
```

```
Net-list summary for /tmp/davidzGit/project/4b_adder_subtractor/LVS/schematic/netlist
count
183      nets
17       terminals
```

```

171      pmos
171      nmos

```

Terminal correspondence points

```

N177      N5      A<0>
N173      N4      A<1>
N169      N6      A<2>
N166      N7      A<3>
N182      N8      B<0>
N181      N9      B<1>
N180      N10     B<2>
N179      N11     B<3>
N175      N3      Ci
N172      N21     Co
N178      N12     S<0>
N174      N13     S<1>
N171      N14     S<2>
N168      N15     S<3>
N167      N1      gnd!
N170      N24     op
N176      N0      vdd!

```

Devices in the netlist but not in the rules:
pcapacitor

Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	342	342
total	342	342
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	183	183
total	183	183
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	17	17

Post Layout Simulation

