 


Introduction to VLSI Final Report

11 December 2013

*By:
Rebecca Curtis
Kancy Robison
David Zemon
Eric Pyle
Will Roussin*

Layout Design



Total Area

$$Area = 175.59 \mu m \cdot 169.335 \mu m = 29,733 \mu m^2$$

Total Power Consumption

$$P = 1.8 \cdot (V_{dd} + \sum_{i=0}^3 A_i + \sum_{i=0}^3 B_i + \sum_{i=0}^2 Op_i + C_i) = 12.6135 mW$$

Worst Case Propagation Delay

For worst case propagation delay, we chose to use the following input conditions:

$$A = 1111$$

$$B = 1111$$

$$C_i = 1$$

$$Op = 100(Add)$$

$$T = 10ns$$

$$t_{rise} = 10ps$$

This yielded a worst case delay of $t_p = 795ps$.